

Computer Organization and Architecture

Course Design



Southeast University
School of Information Science and
Technology

Author: WU YX

Student Number: 040193xx

Project Name: A Parallel Output Controller(POC)

Date: March 23, 2022

Contents

1. Purpose	-----	3
2. Tasks	-----	2
3. Design Analysis	-----	4
3.1 Overall Design	-----	5
3.2 Processor Design	-----	5
3.3 POC Design	-----	7
3.4 Printer Design	-----	8
4. Simulation	-----	9
4.1 Input Waveform Design	-----	9
4.2 Simulation Results	-----	10
5. Conclusion	-----	12
6. Discussion	-----	12
7. Appendix(Source Code)	-----	13

1.Purpose

The purpose of this project is to design and simulate a parallel output controller (POC) which acts an interface between system bus and printer. The Xilinx Vivado is adopted for simulation.

2. Tasks

POC is one of the most common I/O modules, namely the parallel output controller. It plays the role of an interface between the computer system bus and the peripheral (such as a printer or other output devices).

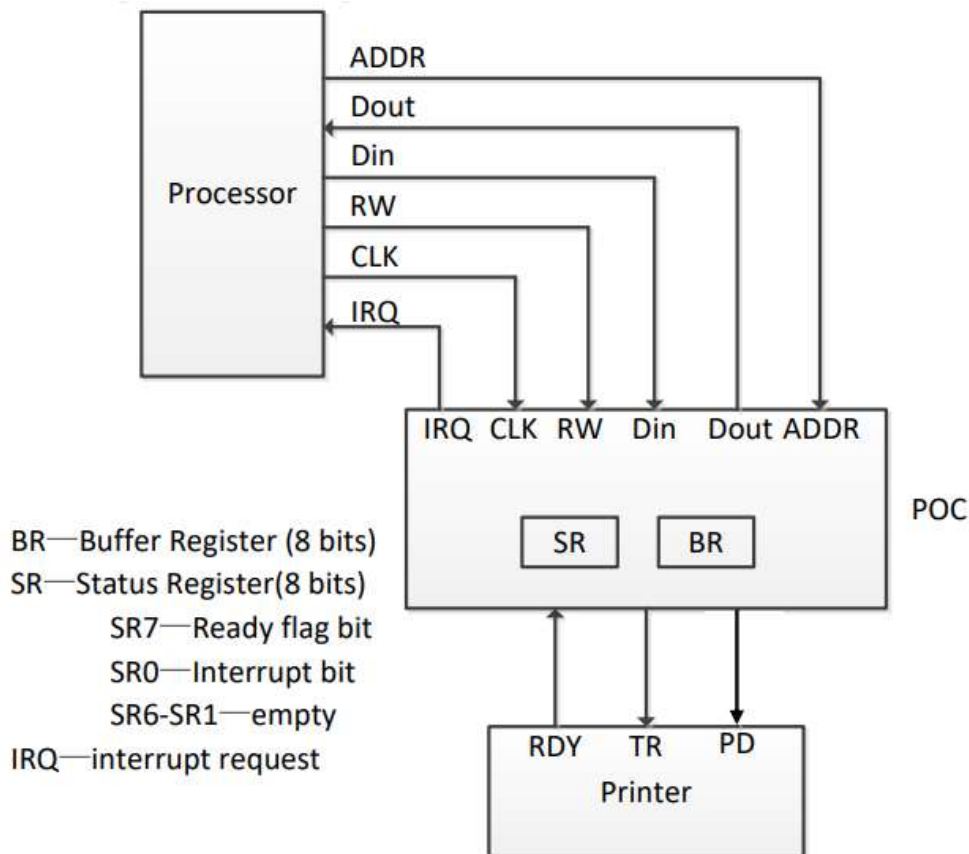


Figure 1 Printer Connection

Figure 1 shows the connecting of a printer to the system bus through the POC. The communication between POC and the printer is controlled by a “handshake” protocol illustrated in Figure 2.

The handshaking process is described as follows: When the printer is

 


Figure 2 The handshake timing diagram between POC and the printer

ready to receive a character, it holds $RDY=1$. The POC then hold a character at PD (parallel data) port and generate a pulse at the port TR (transfer request). The POC will change TR to 0 when detecting printer has respond TR, i.e., RDY has been changed from 1 to 0. When detecting the effective TR signal, the printer will change RDY to 0, take the character at PD and hold the RDY at 0 until the character has been printed (e.g. 5 or 10ms), then set $RDY=1$ again when it is ready to receive the next character. (Suppose the printer has only a one character “buffer” register, so that each character must be printed before the next character is sent).

The buffer register BR is used to temporarily hold a character sent from the processor, which character will be transferred to the printer later. The status register SR is used for two control functions: SR7 serves as a ready flag to indicate POC is ready or not to receive a new character from the processor, and SR0 is used to enable the interrupt requests sent by POC. In in interrupt mode, If $SR0=1$, then POC will send an interrupt request signal to processor when it is ready to receive a character (i.e., when $SR7=1$). If $SR0=0$, then POC will not interrupt. The other bits of SR are not used and empty.

3. Design Analysis

3.1 Overall Design

To adopt modular design , the author designed four independent modules first, namely, Top, Processor, POC and Printer. In Top module, We

providing the whole system with necessary inputs, including clk, modest, reset, and receives the printer output from the system by instantiating the three modules. The connections of all the modules is shown in figure3.

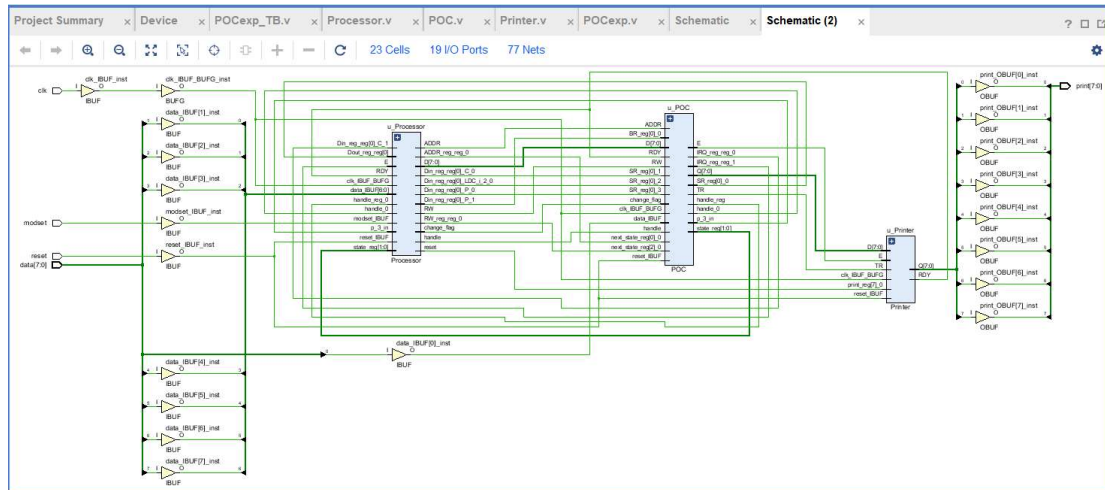


Figure 3 Top Module schematic

3.2 Processor Design

```

23 module Processor(
24     output ADDR, //控制SR还是BR, 1是BR
25     input [7:0]Dout,
26     output [7:0]Din,
27     output RW, //控制读写, 1是cpu向外写
28     input clk,
29     input IRQ, //IRQ为0代表中断请求
30     input reset,
31     input modset, //1中断0查询
32     input [7:0]data
33
34 );

```

Signal Explanations:

Input

[7:0]Dout

Data which is read from POC

[7:0]data

Input data, waiting to be written to POC

clk

Clock signal

IRQ

Interrupt signal read from POC, 0 implies enabled

modset

Change modes from the outside, 1 for interrupt

reset

0 for restart, coordinates with modset


Output

ADDR	Address select control, 1 for BR, 0 for SR
RW	Read or write control, 1 for write into POC
[7:0]Din	Data to be written into POC

Besides, I've designed two internal registers to meet certain functions.

reg handle	a flag that indicates if the written operation has been done by CPU in one circle.
reg change_flag	1 clock time delay which helps the mod change

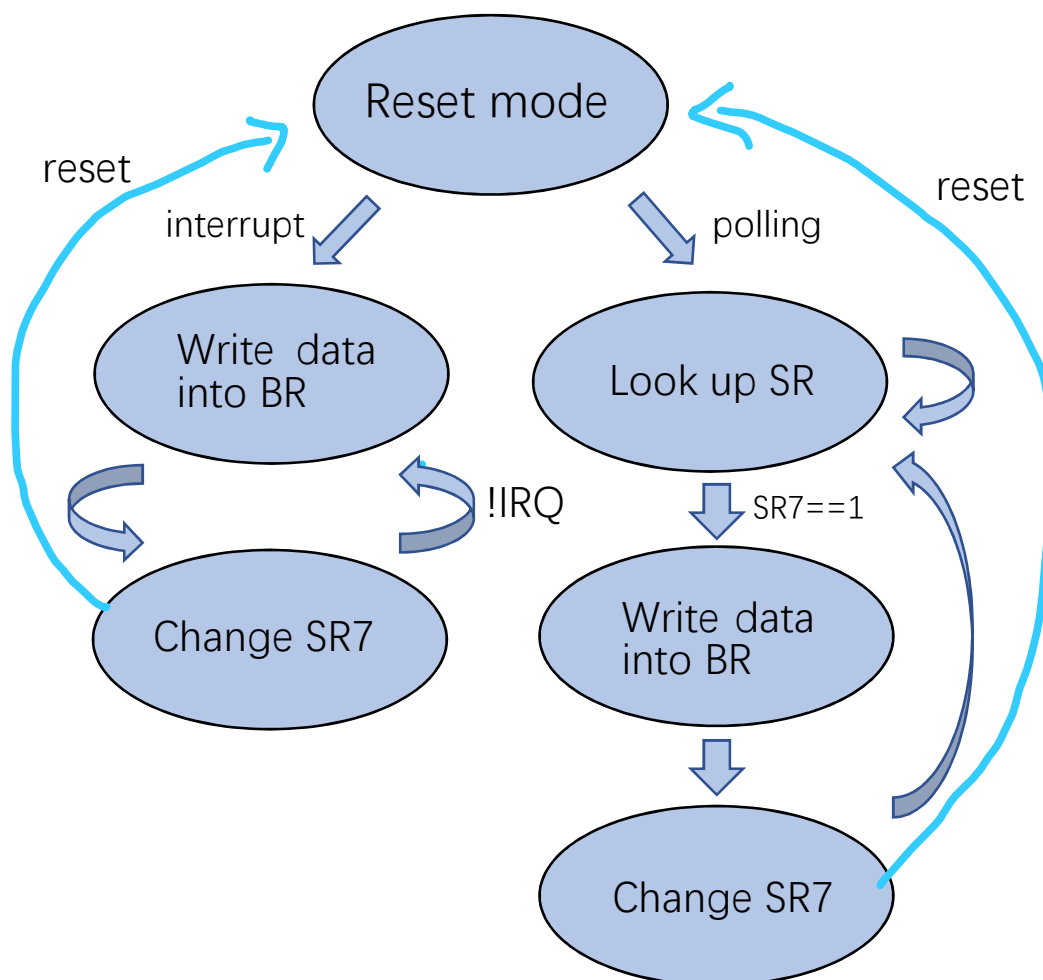For the purpose of the design is to simulate a POC instead of a CPU, we use if-else branches to depict the logic instead of a FSM.



3.3 POC Design

```
23 module POC(  
24     input clk,  
25     output IRQ,  
26     input RW,  
27     input [7:0]Din,  
28     output [7:0]Dout,  
29     input ADDR,  
30     input RDY,  
31     input reset,  
32     // input mod, //1中断0查询  
33     output TR,  
34     output [7:0]PD  
35 )
```

Signal Explanations:

Input

[7:0]Din	Data from CPU.
RW	Input data, waiting to be written to POC
clk	Clock signal
RDY	Ready flag from Printer, 1 for ready
ADDR	Address select control, 1 for BR, 0 for SR
reset	0 for restart


Output

TR	Impulse which activates Printer
IRQ	Interrupt flag, 0 for interrupt
[7:0]PD	Data to be sent to Printer
[7:0]Dout	Data to be sent to CPU

The simulation of POC adopts finite state machine.

```
parameter state1= 3'b000;      start  
parameter state2= 3'b001;      Interrupt
```

 parameter state3= 3'b010; Polling
 parameter state4= 3'b011; handshake after polling
 parameter state5= 3'b100; handshake after interrupt
 parameter state6= 3'b101; refresh SR
 SR1:10000000 SR2:00000000
 SR3:10000001 SR4:00000001



Inside state2 and state3, if-else branches are used to communicate with CPU according to the content of RW and ADDR.

Inside state4 and state5, if RDY==1, POC will activate TR and send data to printer, SR7 is also reset to 1.

3.4 Printer Design

```

23 module Printer(
24     input clk,
25     input TR,
26     input [7:0]PD,
27     input reset,
28     output RDY,
29     output [7:0]PRINT
  
```


Signal Explanations:

Input

[7:0]PD	Data from POC
TR	If TR==1, start receiving data
clk	Clock signal
reset	0 for restart

Output

[7:0]PRINT	Output the received data
RDY	Ready flag for POC

In this module, logic is rather clear, it just needs to receive data and print. A waiting flag and a counter is set to simulate print delay.

4. Simulation

4.1 Input Waveform Design


```
55 begin
56     data=8'b10100101; //第一个data
57     reset=1; //先重开
58     modset=1; //先中断
59     #(JUMP);
60     reset=0; //边沿触发
61     #(JUMP);
62     reset=1;
63
64     #(PERIOD*20);
65     data=8'b11110000; //第2个data
66     #(PERIOD*20);
67     data=8'b00001111; //第3个data
68     #(PERIOD*20);
69
70     reset=0;
71     modset=0;
72     #(JUMP);
73     reset=1;
74     // #(PERIOD*20);
75     // data=8'b00110011; //第4个data
76     #(PERIOD*40);
77     data=8'b11000011; //第4data
78
79     reset=0; //切换
80     modset=1;
81     #(JUMP);
82     reset=1; //边缘触发
83     #(PERIOD*40);
```

Core of the testbench is shown here. It can be concluded into 3 periods.

- 1) Data=10100101(a5)->11110000(f0) ->00001111(0f) interrupt-mode
- 2) Data=00001111(0f) ->11000011(c3) polling-mode
- 3) Data=11000011(c3) interrupt mode


The whole simulation waveform is shown below.

4.2 Simulation Results

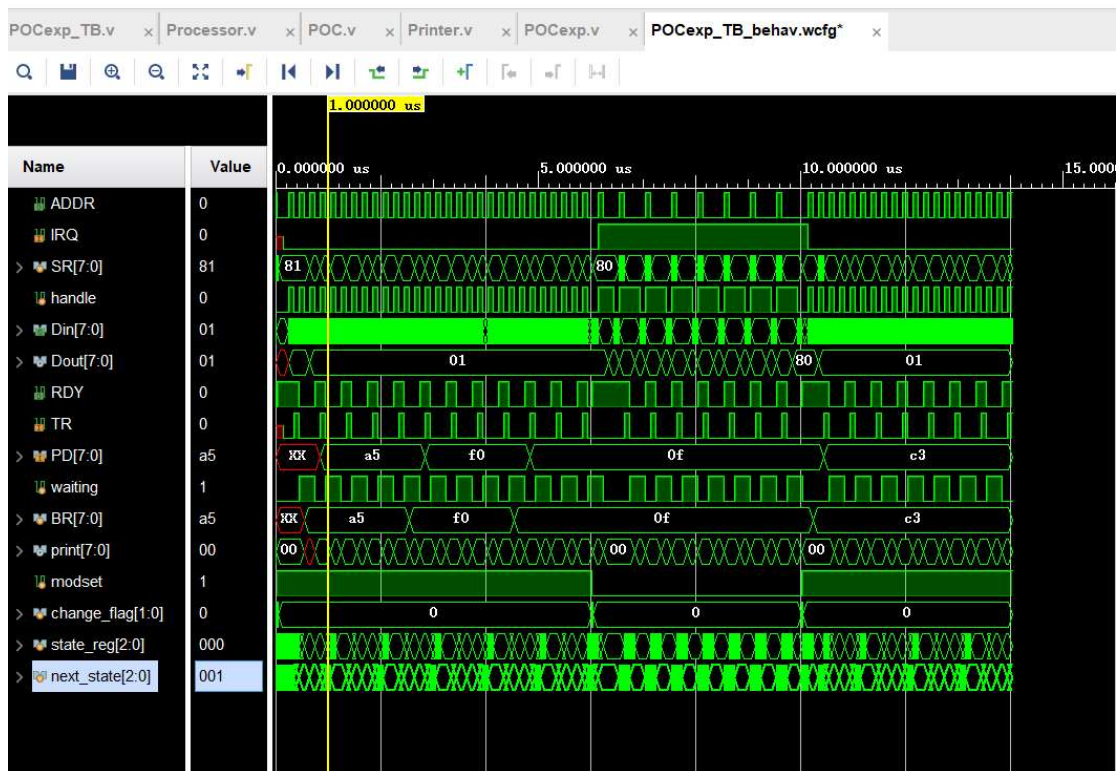

We can clearly figure out that it experienced 3 period of different modes by observing IRQ. We can also clearly figure out that the transmitted data has four different values by observing PD.

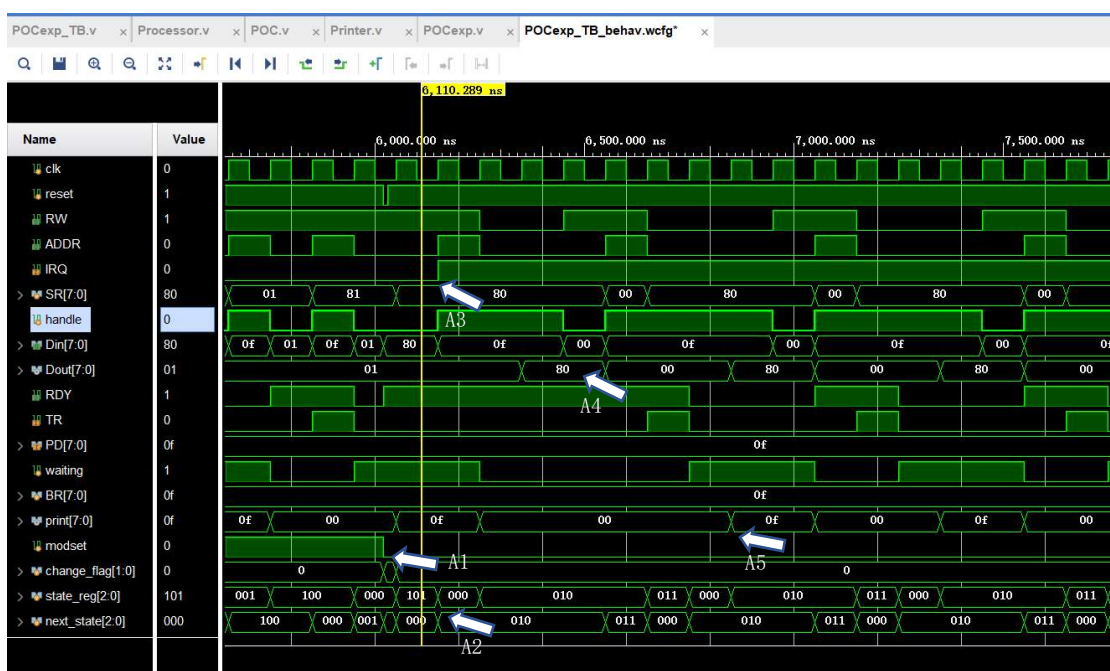Let's further discuss the waveforms by focusing on the two moments when two modes alters each other.



1) The first time of mode changes


A1: At this special moment, we can see that modset changes from 1 to 0, which means from interrupt mode to polling mode.

A2: Here we notice that after reset, the fsm in POC restart from state6, it reads SR set by CPU, and jumps to state3 then state4.

A3: First RW=1, ADDR=0, CPU writes 10000000 through port Din to SR. Then SR=80'h and IRQ turns to 1.

A4: In polling mode, every time CPU writes something to POC, it first checks if POC is ready through port Dout. Hence we can see a loop of 80 and 00 in the value of Dout

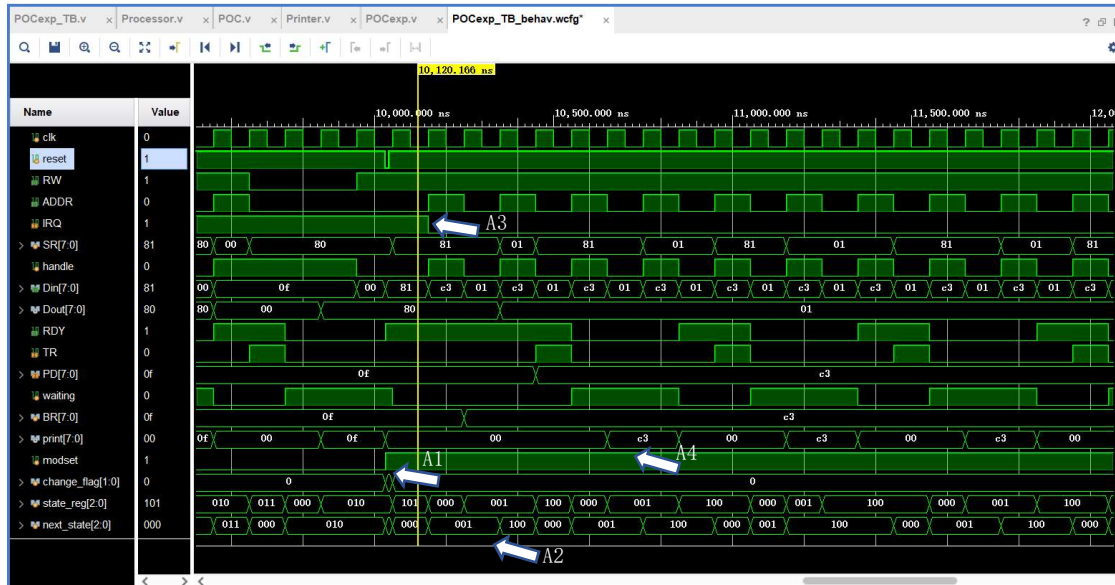A5: The printer is designed to give 00000000 when not printing, when printing, it costs 3 clocks as we can see here.



2) The second time of mode changes

A1: At this special moment, we can see that modset changes from 0 to 1, which means from polling mode to interrupt mode.

A2: Here we notice that after reset, the fsm in POC restart from state6, it reads SR set by CPU, and jumps to state2 then state5.

A3: First RW=1, ADDR=0, CPU writes 10000001 through port Din to SR. Then SR=81'h and IRQ turns to 0.

A4: At this moment, the author intentionally changes input data and mod at the same time to test the robustness of the design. We can find out that the output data also changed from 0f'h to c3'h after reset signal.

5. Conclusion

1. From the this Design, I've recognized that POC is of great significant in the communication between CPU and I/O. It not only plays a role as a buffer, but adjusts the data exchanging rate as well.
2. A matched time flow, which leads to better synchronousness for every parts of a computer system is unavoidable. Proper time sequencing skills help accelerates the rate of I/O stream.
3. In computer system, an important concept is that each time when an operation is done, a signal should be emitted to inform interfaces connected to it. Only then a machine can indeed work as a whole.

6. Discussion

1. Compared to the vast modern computer design strategies, this POC design not a big deal to be discussed. We also have many other I/O mechanisms like DMA and so on. But it doesn't mean this project is meaningless to us. By building the whole system on my own, I've improved my Verilog skills and objectified my recognition to Computer architecture.
2. When coding, I made several mistakes. For example, there was no schematic after synthesis. And I finally found out that this is because I hadn't set an output at TOP level.

Another important concept I've learned from this project is the difference of Finite State Machines, commonly we adopt the 3 segments FSM, but here I adjusted the architecture to fit my design.
3. If there is flaw in this design, I guess the biggest one is its efficiency.

Actually I intentionally made the POC and the Processor two pipelines.
 Their states change with clock, but there are sometimes that the change of
 states maybe paralleled but I limited it to linear to keep a stable system.

4. Thanks for reading

6. Appendix

```

module POCexp(
    input clk,
    input reset,
    input modset,
    input [7:0]data,
    output [7:0]print
);

    wire ADDR;
    wire TR;
    wire RW;
    wire IRQ;
    wire RDY;
    wire [7:0]Din;
    wire [7:0]Dout;
    wire [7:0]PD;

    Processor u_Processor(
        .ADDR(ADDR),//控制SR还是
        BR, 1是BR
        .Dout(Dout[7:0]),
        .Din(Din[7:0]),
        .RW(RW),//控制读写, 1是cpu向
        外写
        .clk(clk),
        .IRQ(IRQ),//IRQ为0代表中断请求
        .reset(reset),
        .modset(modset),
        .data(data[7:0])
    );

    POC u_POC(
        .clk(clk),
        .IRQ(IRQ),
        .RW(RW),
        .Din(Din[7:0]),
        .Dout(Dout[7:0]),
        .ADDR(ADDR),
        .RDY(RDY),
        .TR(TR),
        .PD(PD[7:0]),
        .reset(reset)
    );

    Printer u_Printer(
        .clk(clk),
        .TR(TR),
        .PD(PD[7:0]),
        .RDY(RDY),
        .PRINT(print[7:0]),
        .reset(reset)
    );
endmodule

module Processor(
    output ADDR,//控制SR还是BR,
    1是BR
    input [7:0]Dout,
    output [7:0]Din,
    output RW,//控制读写, 1是cpu向
    外写
    input clk,
    input IRQ,//IRQ为0代表中断请求
    input reset,
    input modset,//1中断0查询
    input [7:0]data

```

```

);

reg ADDR_reg;
reg RW_reg;
reg [7:0]Din_reg;
reg handle=0;//用于判别cpu是否写入br
//reg check=0;//判别查询模式是否查过
//reg [7:0]data=8'b10100101;
reg [1:0]change_flag=2'b00;//模式切换
时空过1slot

always @(negedge reset or posedge clk)
begin
    if(!reset)
    begin
        change_flag<=2'b01;
        if(modset)//如果中断开局
        begin
            ADDR_reg<=0;//写sr
            RW_reg<=1;
            Din_reg<=8'b10000001;
            handle<=0;
        end
        else
        begin//查询模式开局
            ADDR_reg<=0;//写sr
            RW_reg<=1;
            Din_reg<=8'b10000000;
            handle<=0;
        end
    end
    else
    //    begin

//    end
//end
//        //reset根据mod重置为默认
//always @(posedge clk)
//    begin
//        if(change_flag==2'b01)
//        begin
//            //空置时隙
//            change_flag<=2'b00;
//        end
//        else if(change_flag==2'b00)
//        begin
//            if(!IRQ)//中断请求
//            begin
//                if(handle==0)
//                begin
//                    ADDR_reg<=1;
//                    RW_reg<=1;
//                    Din_reg<=data;//写入data
//                    handle<=1;
//                end
//                else
//                begin
//                    ADDR_reg<=0;
//                    RW_reg<=1;
//                    Din_reg<=8'b00000001;//SR0=1,SR7=0
//                    ;
//                    handle<=0;//sr
//                    处理完毕
//                end
//            end
//            /*
//            else
//            if(RW&&Dout==8'b00000001)//没准备好
//            好
//            begin
//                RW_reg=0;
//            end
//            */
//            else if(IRQ)//查询
//            begin
//                if(Dout==8'b10000000)
//                //查询sr7
//                begin
//                    if(handle==0)
//                    begin
//                        RW_reg

```

```

<= 1;

ADDR_reg <= 1;

Din_reg<=data;

handle<=1;

                                end
                                else
                                begin//置sr7=0
                                    RW_reg
                                );
                                output IRQ,
                                input RW,
                                input [7:0]Din,
                                output [7:0]Dout,
                                input ADDR,
                                input RDY,
                                input reset,
                                // input mod,//1中断0查询
                                output TR,
                                output [7:0]PD
                                );
                                reg IRQ_reg;
                                reg TR_reg;
                                reg[7:0] PD_reg;
                                reg[7:0] Dout_reg;
                                reg[2:0] state_reg;
                                reg[2:0] next_state=3'b000;
                                reg[7:0] BR;
                                reg[7:0] SR;

                                parameter state1= 3'b000;
                                parameter state2= 3'b001;
                                parameter state3= 3'b010;
                                parameter state4= 3'b011;
                                parameter state5= 3'b100;
                                parameter state6= 3'b101;//重开模式

                                always@(negedge reset or posedge clk)
                                begin
                                    // mod_reg<=mod;//首先载入模式
                                    if(!reset)
                                    begin
                                        next_state=state6;//先读取模式
                                    end
                                    // mod_reg<=0;//默认查询
                                else
                                begin
                                    state_reg=next_state;
                                end
                                end
                                always@(posedge clk)
                                begin
                                    assign ADDR = ADDR_reg;
                                    assign RW = RW_reg;
                                    assign Din = Din_reg;
                                endmodule

                                module POC(
                                    input clk,

```

```

//state_reg=next_state;
case(state_reg)
    state1:
    begin
        TR_reg<=0;//复原TR脉冲
        if(SR==8'b10000001)
        begin
            IRQ_reg<=0;
            next_state<=state2;
        end
    end
else
    if(SR==8'b10000000)
    begin
        IRQ_reg<=1;
        next_state<=state3;
    end
    else
    if(SR==8'b00000000)
    begin
        IRQ_reg<=1;
        next_state<=state4;
    end
    else
    if(SR==8'b00000001)
    begin
        IRQ_reg<=0;
        next_state<=state5;
    end
    else//reset模式尝试
    begin
        next_state<=state6;
    end
end
state2://中断
begin
    if(RW==1&&ADDR==1)
    begin
        BR<=Din;
        //SR<=8'b00000001;
        // next_state=state2;
    end
    else
    if(RW==1&&ADDR==0)
    begin
        SR<=Din;
        Dout_reg<=Din;
        next_state<=state5;
    end
    end
state3://查询
begin
    if(RW==0&&ADDR==0)//读sr
    begin
        Dout_reg<=SR;
        //next_state=state3;
        //next_state
        <=state3;
    end
    else
    if(RW==1&&ADDR==1)//写br
    begin
        BR<=Din;
        //next_state=state3;
        //next_state
        <=state3;
    end
    else
    if(RW==1&&ADDR==0)//写sr
    begin
        SR<=Din;
        Dout_reg<=Din;
        next_state<=state4;
    end
    end
state4://查询后握手
begin
    if(RDY)
    begin
        TR_reg<=1;
        PD_reg<=BR;
        SR<=8'b10000000;
        next_state<=state1;
    end
end
end

```



```

        end
    end
    state5://中断后握手
    begin
        if(RDY)
            begin
                TR_reg<=1;
                PD_reg<=BR;
                SR<=8'b10000001;
                next_state<=state1;
            end
        end
    end
    state6:
    begin
        SR<=Din;
        next_state<=state1;
    end
    default:
        next_state<=state6;
    endcase
end

assign IRQ = IRQ_reg;
assign TR = TR_reg;
assign PD = PD_reg;
assign Dout = Dout_reg;

endmodule

module Printer(
    input clk,
    input TR,
    input [7:0]PD,
    input reset,
    output RDY,
    output [7:0]PRINT
);
reg [7:0]data;//data是转存
reg [7:0]print;//print是等待后打印输出
reg [2:0]counter=3'b000;
//计时器
reg waiting=0;
//写入过程的waiting, 写入时为1

```

```

reg ready;
//RDY的赋值版本

always @(posedge clk or negedge reset)
begin
    if(!reset)
        begin
            print<=0;
            ready<=1;
        end
    else
        begin
            if(TR)
                begin
                    ready<=0;
                    data<=PD;
                    waiting<=1;
                    //如果TR已经触发, 不
                    再接收, 开始等待延时
                end
            else//TR没触发
                begin
                    if(waiting)//如果是等待
                    中
                        begin
                            counter<=counter+1;
                            print<=data;
                            if(counter==3'b010)
                                begin
                                    print<=0;
                                    ready=1;
                                    waiting<=0;
                                    counter<=0;
                                end
                            end
                        end
                    end
                end
            end
        end

    assign RDY = ready;
    assign PRINT = print;
endmodule

```